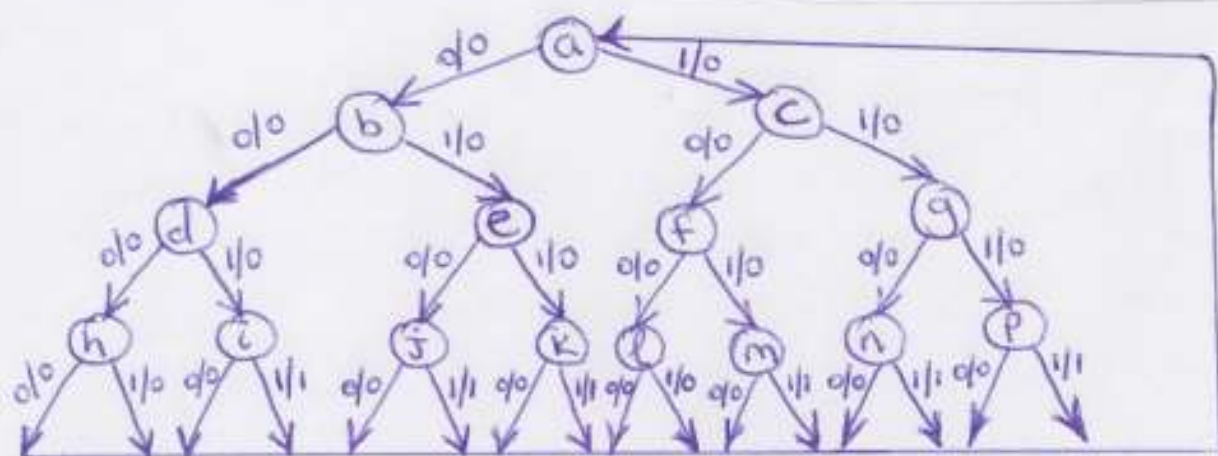


Example: A single-input single-output clocked sequential circuit is to be designed. The circuit will determine whether a string of four consecutive input bits constitute a valid BCD code or not. The output $Z=1$ if the four consecutive bits DO NOT constitute a valid BCD representation, and $Z=0$ otherwise. Least significant bit of the BCD code is applied to the checker input first.

$X \rightarrow \text{BCD checker} \rightarrow Z$ (after the 4th input)



| PS | NS | | Output | |
|----|-----|-----|--------|-----|
| | x=0 | x=1 | x=0 | x=1 |
| a | b | c | 0 | 0 |
| b | d | e | 0 | 0 |
| c | f | g | 0 | 0 |
| d | h | i | 0 | 0 |
| e | j | k | 0 | 0 |
| f | l | m | 0 | 0 |
| g | n | p | 0 | 0 |
| h | a | a | 0 | 0 |
| i | a | a | 0 | 1 |
| j | a | a | 0 | 1 |
| k | a | a | 0 | 1 |
| l | a | a | 0 | 0 |
| m | a | a | 0 | 1 |
| n | a | a | 0 | 1 |
| p | a | a | 0 | 1 |

— State table —

$$P_1 = (a, b, c, d, e, f, g, h, l) \quad (i, j, k, m, n, p)$$

$$P_2 = (a, b, c, h, l) (d, f) (e, g) (i, j, k, m, n, p)$$

$$P_3 = (a, h, l) (b, c) (d, f) (e, g) (i, j, k, m, n, p)$$

$$P_4 = (a) (h, l) (b, c) (d, f) (e, g) (i, j, k, m, n, p)$$

| PS | NS | | Output | |
|----|-----|-----|--------|-----|
| | x=0 | x=1 | x=0 | x=1 |
| a | b | b | 0 | 0 |
| b | d | e | 0 | 0 |
| d | h | i | 0 | 0 |
| e | i | i | 0 | 0 |
| h | a | a | 0 | 0 |
| i | a | a | 0 | 1 |

— Reduced state table —

\Rightarrow h, i must be adjacent
d, e may be adjacent

| | 00 | 01 | 11 | 10 |
|---|----|----|----|----|
| 0 | h | d | b | a |
| 1 | i | e | — | — |

$$h \equiv 000 \quad i \equiv 100$$

$$d \equiv 001 \quad e \equiv 101$$

$$a \equiv 010$$

$$b \equiv 011$$

| PS | NS | | Output | |
|---------|-----|-----|--------|-----|
| | X=0 | X=1 | X=0 | X=1 |
| ABC | ABC | ABC | z | z |
| h → 000 | 010 | 010 | 0 | 0 |
| d → 001 | 000 | 100 | 0 | 0 |
| a → 010 | 011 | 011 | 0 | 0 |
| b → 011 | 001 | 101 | 0 | 0 |
| i → 100 | 010 | 010 | 0 | 1 |
| e → 101 | 100 | 100 | 0 | 0 |

6 states \Rightarrow 3 FFs

3 FFs \Rightarrow 8 states

$$2^3 = 8$$

\therefore 2 unused states:
110 and 111

Design the circuit using one JK FF for A, one RS FF for B and one T FF for C.

| PS | Input | NS | Output | Flip-flop Inputs | | | | |
|-----|-------|-------|--------|------------------|----|----|----|----|
| ABC | X | ABC | z | JA | KA | SB | RB | Tc |
| 000 | 0 | 010 | 0 | 0 | X | 1 | 0 | 0 |
| 000 | 1 | 010 | 0 | 0 | X | 1 | 0 | 0 |
| 001 | 0 | 000 | 0 | 0 | X | 0 | X | 1 |
| 001 | 1 | 100 | 0 | 1 | X | 0 | X | 1 |
| 010 | 0 | 011 | 0 | 0 | X | X | 0 | 1 |
| 010 | 1 | 011 | 0 | 0 | X | X | 0 | 1 |
| 011 | 0 | 001 | 0 | 0 | X | 0 | 1 | 0 |
| 011 | 1 | 101 | 0 | 1 | X | 0 | 1 | 0 |
| 100 | 0 | 010 | 0 | X | 1 | 1 | 0 | 0 |
| 100 | 1 | 010 | 1 | X | 1 | 1 | 0 | 0 |
| 101 | 0 | 100 | 0 | X | 0 | 0 | X | 1 |
| 101 | 1 | 100 | 0 | X | 0 | 0 | X | 1 |
| 110 | 0 | X X X | X | X | X | X | X | X |
| 110 | 1 | X X X | X | X | X | X | X | X |
| 111 | 0 | X X X | X | X | X | X | X | X |
| 111 | 1 | X X X | X | X | X | X | X | X |

— Excitation Table —

Remember :

| PS | NS | J | K |
|----|----|---|---|
| 0 | 0 | 0 | X |
| 0 | 1 | 1 | X |
| 1 | 0 | X | 1 |
| 1 | 1 | X | 0 |

| PS | NS | S | R |
|----|----|---|---|
| 0 | 0 | 0 | X |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | X | 0 |

| PS | NS | T |
|----|----|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

Using the K-map simplification;

| AB \ C | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| 00 | | | 1 | |
| 01 | | | 1 | |
| 11 | X | X | X | X |
| 10 | X | X | X | X |

$$J_A = CX$$

| | | | |
|---|---|---|---|
| X | X | X | X |
| X | X | X | X |
| X | X | X | X |
| 1 | 1 | | |

$$K_A = C'$$

| | | | |
|---|---|---|---|
| 1 | 1 | | |
| X | X | | |
| X | X | X | X |
| 1 | 1 | | |

$$S_B = C'$$

| | | | |
|---|---|---|---|
| | | X | X |
| | | 1 | 1 |
| X | X | X | X |
| | | X | X |


$$R_B = C$$

| | | | |
|---|---|---|---|
| | | 1 | 1 |
| 1 | 1 | | |
| X | X | X | X |
| | | 1 | 1 |

$$T_C = B'C + BC' = B \oplus C$$

| | | | |
|---|---|---|---|
| | | | |
| | | | |
| X | X | X | X |
| | | 1 | |

$$Z = AC'X$$

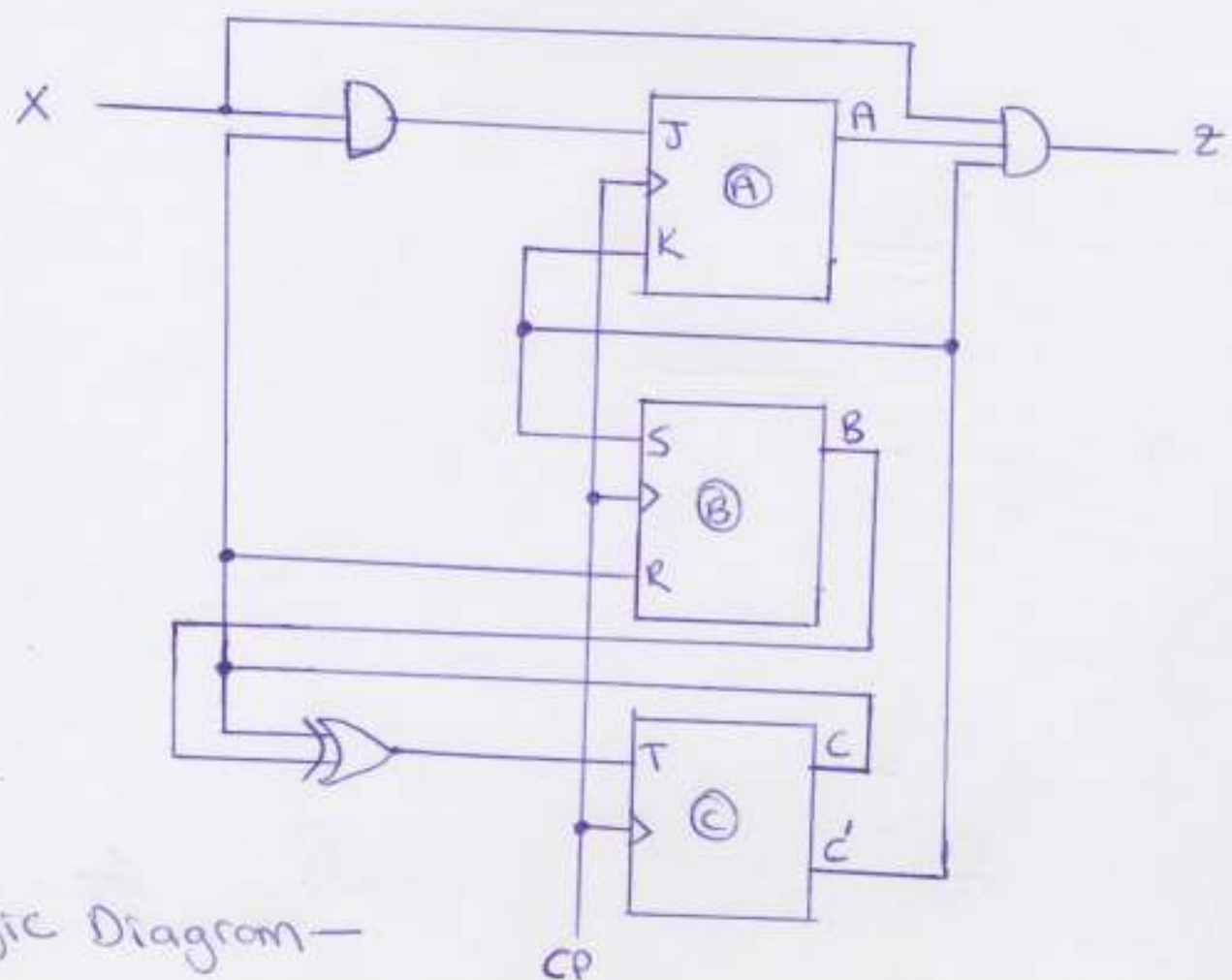

— Logic Diagram —


Example: A sequential circuit with two D flip-flops, A and B; two inputs, x and y; and one output, z, is specified by the following next-state and output equations:

$$A(t+1) = x'y + xA, \quad B(t+1) = x'B + xA, \quad z = B$$

- Draw the logic diagram of the circuit
- Derive the state table
- Derive the state diagram

Solution:

a)

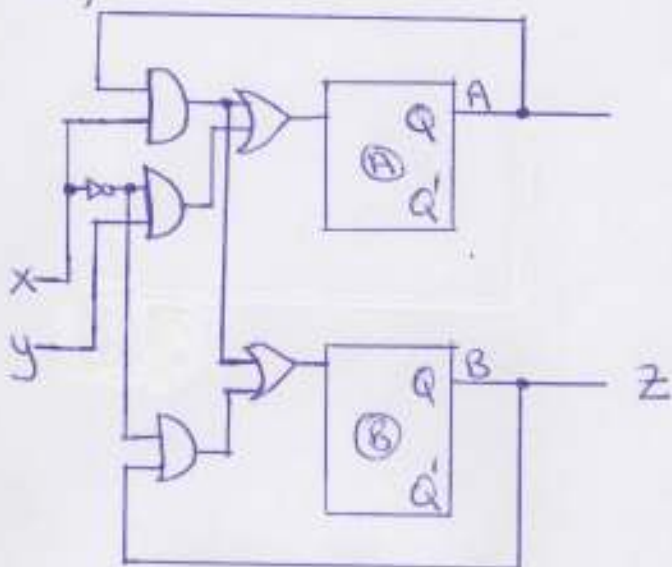

b) $A(t+1): A$

| xy \ AB | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00 | | | | |
| 01 | 1 | 1 | 1 | 1 |
| 11 | | | 1 | 1 |
| 10 | | | 1 | 1 |

B

$B(t+1): B$

| xy \ AB | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00 | | 1 | 1 | |
| 01 | | 1 | 1 | |
| 11 | | | 1 | 1 |
| 10 | | | 1 | 1 |


$z:$

| xy \ AB | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00 | | 1 | 1 | |
| 01 | | 1 | 1 | |
| 11 | | | 1 | 1 |
| 10 | | | 1 | 1 |

| PS | NS | | | | Output | | | |
|----|-------|----|----|----|--------|----|----|----|
| AB | xy=00 | 01 | 11 | 10 | 00 | 01 | 11 | 10 |
| | AB | AB | AB | AB | z | z | z | z |
| 00 | 00 | 10 | 00 | 00 | 0 | 0 | 0 | 0 |
| 01 | 01 | 11 | 00 | 00 | 1 | 1 | 1 | 1 |
| 11 | 01 | 11 | 11 | 11 | 1 | 1 | 1 | 1 |
| 10 | 00 | 10 | 11 | 11 | 0 | 0 | 0 | 0 |

— State table —

c)

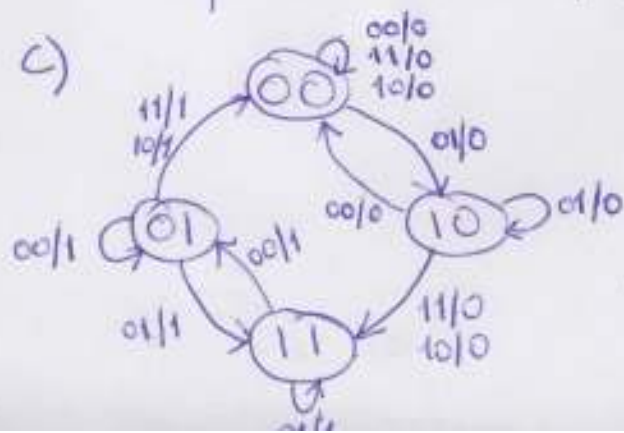

— State diagram —

Example: A sequential circuit has three D flip-flops, A, B, and C, and one input, X. It is described by the following flip-flop input functions:

$$D_A = (BC' + B'C)X + (BC + B'C')X'$$

$$D_B = A$$

$$D_C = B$$

a) Derive the state table

b) Draw two state diagrams: one for $x=0$ and the other for $x=1$

a) Next state equations:

$$A(t+1) = D = XBC' + XB'C + X'BC + X'B'C', \quad B(t+1) = A, \quad C(t+1) = B$$

| XA \ BC | | B | | | |
|---------|----|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| A | 00 | 1 | | 1 | |
| | 01 | 1 | | 1 | |
| | 11 | | 1 | | 1 |
| | 10 | | 1 | | 1 |

$A(t+1)$

| XA \ BC | | | | | |
|---------|----|---|---|---|---|
| | | | | | |
| A | 00 | | | | |
| | 01 | 1 | 1 | 1 | 1 |
| | 11 | 1 | 1 | 1 | 1 |
| | 10 | | | | |

$B(t+1)$

| XA \ BC | | | | | |
|---------|----|--|--|---|---|
| | | | | | |
| A | 00 | | | 1 | 1 |
| | 01 | | | 1 | 1 |
| | 11 | | | 1 | 1 |
| | 10 | | | 1 | 1 |

$C(t+1)$

| PS ABC | NS | |
|-----------|------------|------------|
| | x=0 ABC | x=1 ABC |
| 000 | 100 | 000 |
| 001 | 000 | 100 |
| 010 | 001 | 101 |
| 011 | 101 | 001 |
| 100 | 110 | 010 |
| 101 | 010 | 110 |
| 110 | 011 | 111 |
| 111 | 111 | 011 |

