


## COMPUTER ARCHITECTURE EXPERIMENT – 3

### Implementation of Synchronous Sequential Circuits

**Aim:** In this experiment, students will be introduced to the concept of sequential circuits and implement a 2-bit Counter.
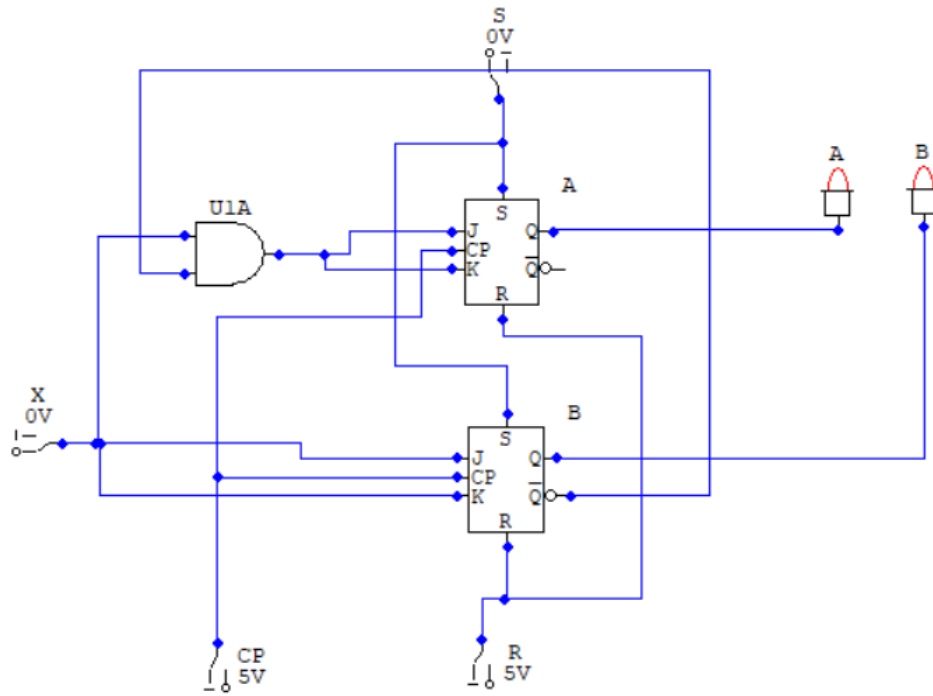
#### Experimental Work:

*Given the following sequential circuit:*



X

## CP

1. Draw the logic diagram of the given sequential circuit in Circuit Maker 6.0.

a) Implement your inputs as logic switches.

*Devices → Hotkeys2 → logic switch*

b) Implement your circuit using logic gates and JK- Flip Flops (4027).

*(You can search devices from devices → search)*

c) Implement your outputs as logic displays.

*Devices → Hotkeys1 → logic display*

2. Run your circuit and complete the following state table:

Present State			Next State			
A(t)	B(t)	x	A(t+1)	B(t+1)		
0	0	0	0 A(t)	0 B(t)	A(t)	B(t)
0	0	1	1	1	A(t+1)	B(t+1)
0	1	0	0 A(t)	1 B(t)	A(t)	B(t)
0	1	1	0	0	A(t+1)	B(t+1)
1	0	0	1 A(t)	0 B(t)	A(t)	B(t)
1	0	1	0	1	A(t+1)	B(t+1)
1	1	0	1 A(t)	1 B(t)	A(t)	B(t)
1	1	1	1	0	A(t+1)	B(t+1)

3. Supply your flip-flop input equations:

ID: 21707346

Name/Surname: Barış Karapelit

2. Run your circuit and complete the following state table:

Present State			Next State			
A(t)	B(t)	x	A(t+1)	B(t+1)		
0	0	0	0	0	A(t)	B(t)
0	0	1	1	1	A(t+1)	B(t+1)
0	1	0	0	1	A(t)	B(t)
0	1	1	0	0	A(t+1)	B(t+1)
1	0	0	1	0	A(t)	B(t)
1	0	1	0	1	A(t+1)	B(t+1)
1	1	0	1	1	A(t)	B(t)
1	1	1	1	0	A(t+1)	B(t+1)

3. Supply your flip-flop input equations:

$$T_A = A \cdot B' \quad T_B = A$$

$$Q_{(t+1)} = T \cdot Q' + T' \cdot Q$$

$$A_{(t+1)} = T_A \cdot A' + T_A' \cdot A$$

$$A_{(t+1)} = A \cdot B' \cdot A' + (A \cdot B')' \cdot A$$

$$A_{(t+1)} = 0 + (A' + B) \cdot A$$

$$A_{(t+1)} = A' \cdot A + A \cdot B$$

$$A_{(t+1)} = 0 + A \cdot B$$

$$A_{(t+1)} = A \cdot B$$

$$B_{(t+1)} = T_B \cdot B' + T_B' \cdot B$$

$$B_{(t+1)} = A \cdot B' + A' \cdot B$$

$$B_{(t+1)} = A \oplus B$$