

REVIEW OF LOGIC DESIGN

BOOLEAN ALGEBRA

The Boolean algebra is an algebra dealing with binary variables and logic operations.

A Boolean expression is an algebraic expression formed by using binary variables, the constants 1 and 0, the logic operation symbols and parenthesis.

Basic Properties and Theorems:

Closure w.r.t. $+$: $x, y \in B \rightarrow x + y \in B$

Closure w.r.t. \cdot : $x, y \in B \rightarrow x \cdot y \in B$

1- a) $A + 0 = A$	$0 \cdot 0 = 0$
b) $A \cdot 1 = A$	$0 + 0 = 0$
2- a) $A + 1 = 1$	$1 \cdot 1 = 1$
b) $A \cdot 0 = 0$	$1 + 1 = 1$
3- a) $A + A = A$	$1 \cdot 0 = 0$
b) $A \cdot A = A$	$0 \cdot 1 = 0$
4- a) $A + \bar{A} = 1$	$0 + 1 = 1$
b) $A \cdot \bar{A} = 0$	$1 + 0 = 1$
5- a) $\bar{\bar{A}} = A$	
b) $\overline{(\bar{A})} = A$	

6- a) $A \cdot B = B \cdot A$ b) $A + B = B + A$	Commutative
7- a) $(A + B) + C = A + (B + C)$ b) $(A \cdot B) \cdot C = A \cdot (B \cdot C)$	Associative
8- a) $A \cdot (B + C) = A \cdot B + A \cdot C$ b) $A + B \cdot C = (A + B) \cdot (A + C)$	Distributive
9- a) $A + A \cdot B = A$ b) $A \cdot (A + B) = A$	Absorbtion
10- a) $A + \bar{A} \cdot B = A + B$ b) $A \cdot (\bar{A} + B) = A \cdot B$	Common Identities

De Morgan's Theorem:

a) $\overline{A + B} = \bar{A} \cdot \bar{B}$
b) $\overline{A \cdot B} = \bar{A} + \bar{B}$

LOGIC OPERATIONS

There are 2 to the power of 2^n different combinations (functions) for n binary variables. So, for $n = 2$, there are $2^4 = 16$ Boolean functions:









x	y	F ₀	F ₁	F ₂	F ₃	F ₄	F ₅	F ₆	F ₇	F ₈	F ₉	F ₁₀	F ₁₁	F ₁₂	F ₁₃	F ₁₄	F ₁₅
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

1. Two functions that produce a constant 0 or 1: F₀, F₁₅.
2. Four functions with unary operations complement and transfer: F₃, F₅, F₁₀, F₁₂.
3. Ten functions with binary operators that define 8 different operations: AND, OR, NAND, NOR, XOR, XNOR (EQUIVALANCE), Inhibition, Implication.

Boolean Expressions for the 16 Functions of Two Variables

Boolean Functions	Operator Symbol	Name	Comments
$F_0 = 0$		Null	Binary constant 0
$F_1 = xy$	$x \cdot y$	AND	x and y
$F_2 = xy'$	x/y	Inhibition	x , but not y
$F_3 = x$		Transfer	x
$F_4 = x'y$	y/x	Inhibition	y , but not x
$F_5 = y$		Transfer	y
$F_6 = xy' + x'y$	$x \oplus y$	Exclusive-OR	x or y , but not both
$F_7 = x + y$	$x + y$	OR	x or y
$F_8 = (x + y)'$	$x \downarrow y$	NOR	Not-OR
$F_9 = xy + x'y'$	$(x \oplus y)'$	Equivalence	x equals y
$F_{10} = y'$	y'	Complement	Not y
$F_{11} = x + y'$	$x \supset y$	Implication	If y , then x
$F_{12} = x'$	x'	Complement	Not x
$F_{13} = x' + y$	$x \supset y$	Implication	If x , then y
$F_{14} = (xy)'$	$x \uparrow y$	NAND	Not-AND
$F_{15} = 1$		Identity	Binary constant 1

LOGIC GATES

Name	Graphic symbol	Algebraic function	Truth table															
AND		$F = x \cdot y$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	0	0	1	0	1	0	0	1	1	1
x	y	F																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$F = x + y$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	1
x	y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
Inverter		$F = x'$	<table><tr><th>x</th><th>F</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	x	F	0	1	1	0									
x	F																	
0	1																	
1	0																	
Buffer		$F = x$	<table><tr><th>x</th><th>F</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	x	F	0	0	1	1									
x	F																	
0	0																	
1	1																	
NAND		$F = (xy)'$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	1	0	1	1	1	0	1	1	1	0
x	y	F																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR		$F = (x + y)'$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	0
x	y	F																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
Exclusive-OR (XOR)		$F = xy' + x'y$ $= x \oplus y$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	0
x	y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
Exclusive-NOR or equivalence		$F = xy + x'y'$ $= (x \oplus y)'$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	1
x	y	F																
0	0	1																
0	1	0																
1	0	0																
1	1	1																

XOR and XNOR

2-input XOR – XNOR:

3-input XOR – XNOR:

Properties of XOR Function:

$$x \oplus 0 = x$$

$$x \oplus 1 = x'$$

$$x \oplus x = 0$$

$$x \oplus x' = 1$$

$$x \oplus y' = x' \oplus y = (x \oplus y)'$$

Prove that:

a) $(x \text{ XOR } y \text{ XOR } z)' = (x \text{ XNOR } y \text{ XNOR } z)$

b) $(x \text{ XNOR } y \text{ XNOR } z) = ((x \text{ XOR } y) \text{ XNOR } z)$