

## CHAPTER - 4 -


### TRANSIENTS

The time varying currents and voltages resulting from the sudden application of sources, possibly due to switching, are called transients.

#### First-Order RC Circuits

Discharging of a capacitance


Consider the following circuit

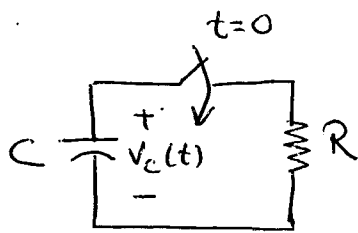

Capacitance charged to  $V_i$  prior to  $t=0$ . ( $V_C(0)=V_i$ )

At  $t=0$ , the switch closes and current flows through the resistor, discharging the capacitor.

$t > 0$

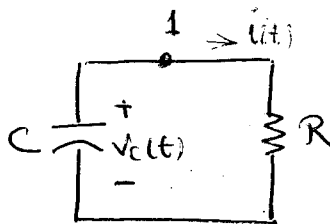

$$\frac{V_C(t)}{R} = -C \frac{dV_C(t)}{dt} \Rightarrow \frac{C dV_C(t)}{dt} + \frac{V_C(t)}{R} = 0$$

$$i(t) = \frac{V_C(t)}{R} \quad (\text{Ohm's law})$$

$$i(t) = -C \frac{dV_C(t)}{dt}$$

$$RC \frac{dV_c(t)}{dt} + V_c(t) = 0 \quad (1)$$

The above equation indicates that the solution for  $V_c(t)$  must be function that has the same form as its first derivative.

$$V_c(t) = K e^{st} \quad (2)$$

in which  $K$  and  $s$  are constants to be determined

Substitute (2) into (1)

$$RC \frac{d}{dt} (K e^{st}) + K e^{st} = 0$$

$$RC \cancel{K} \cancel{s} e^{st} + \cancel{K} e^{st} = 0$$

$$s = -\frac{1}{RC}$$

$$V_c(t) = K e^{-t/RC}$$


The voltage across the capacitor can not change instantaneously when the switch closes. The voltage across the capacitor must be continuous. Thus

$$V_c(0^-) = \underbrace{V_c(0^+)} = V_i$$

↳ voltage immediately after the switch closes.

$$V_c(0^+) = V_i = K e^0 = K$$

$$V_c(t) = V_i e^{-t/RC}$$

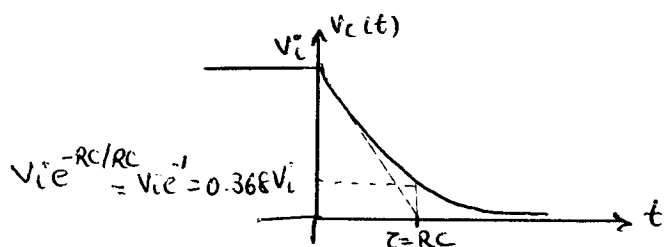


The time interval  $\tau = RC$  is called the time constant.

Question:


The switch in the following circuit has been in position x for a long time. At  $t=0$ , the switch moves instantaneously to position y. Find

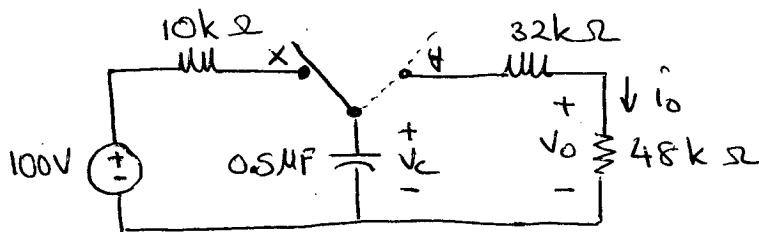- (a)  $V_c(t)$  for  $t \geq 0$
- (b)  $V_o(t)$  for  $t \geq 0^+$
- (c)  $i_o(t)$  for  $t \geq 0^+$
- (d) the total energy dissipated in the  $48\text{ k}\Omega$  resistor.




Solution:


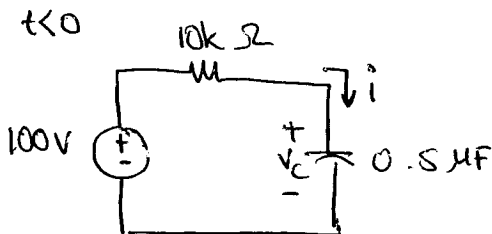
- (a) Because the switch has been in position x for a long time, the  $0.5\text{ }\mu\text{F}$  capacitor will charge to  $100\text{V}$ .



$$i = C \frac{dV_c}{dt} = 0$$

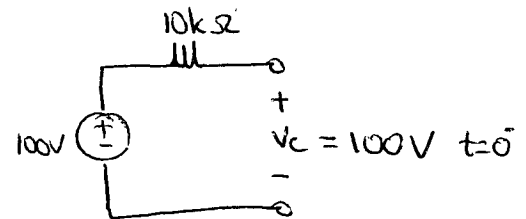

$t \geq 0$

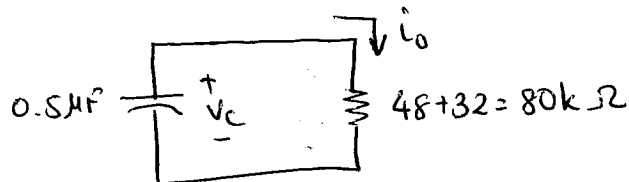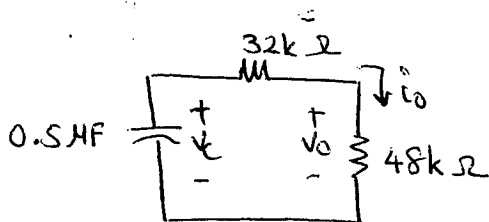


$$V_c(t) = V_i e^{-t/RC}$$

$$V_c(0^-) = V_c(0^+) = 100 = V_i e^{-0/RC} \Rightarrow V_i = 100$$

$$V_c(t) = 100 e^{-25t} \text{ V}, \quad t \geq 0 \quad 1/RC = 1/(0.5 \times 10^{-6})(80 \times 10^3) = 25$$

(b)

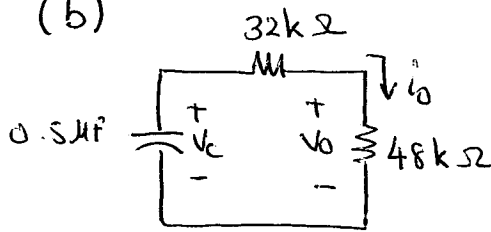

$$\begin{aligned}
 V_0(t) &= V_c(t) \frac{48k}{32k+48k} \\
 &= \frac{48}{80} 100 e^{-25t} \\
 &= 60 e^{-25t} \text{ V } t \geq 0^+
 \end{aligned}$$

$$(c) \quad i_0(t) = \frac{V_0(t)}{48k} = \frac{60 e^{-25t}}{48 \times 10^3}$$

$$i_0(t) = 1.25 \times 10^{-3} e^{-25t}$$

$$i_0(t) = 1.25 e^{-25t} \text{ mA } t \geq 0^+$$

(d) The power dissipated in the 48 kΩ resistor

$$\begin{aligned}
 P_{48k\Omega}(t) &= i_0^2(t) (48 \times 10^3) = (1.25 \times 10^{-3} e^{-25t})^2 (48 \times 10^3) \\
 &= 75 \times 10^{-3} e^{-50t} \\
 &= 75 e^{-50t} \text{ mW}
 \end{aligned}$$

The total energy dissipated

$$\begin{aligned}
 W_{48k\Omega} &= \int_0^{\infty} P_{48k\Omega}(t) dt \\
 &= \int_0^{\infty} 75 \times 10^{-3} e^{-50t} dt
 \end{aligned}$$


$$= \frac{-75 \times 10^{-3}}{50} \left[ e^{-50t} \right]_0^{\infty}$$

$$= -1.5 \times 10^{-3} (e^{-\infty} - e^{-0}) = 1.5 \times 10^{-3} = 1.5 \text{ mJ}$$

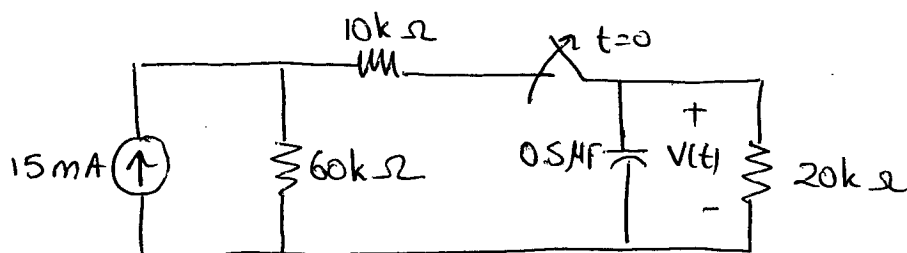
## Home Exercise

The switch in the following circuit has been closed for a long time and is opened at  $t=0$ . Find

- the initial value of  $v(t)$
- the time constant for  $t > 0$
- the numerical expression for  $v(t)$  after the switch has been opened
- the initial energy stored in the capacitor
- the length of time required to dissipate 75% of the initial stored energy.



Solution:

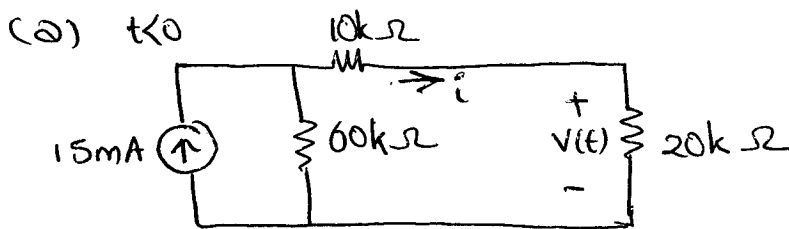


$$i = 15 \times 10^{-3} \frac{60 \times 10^3}{60 \times 10^3 + 10 \times 10^3 + 20 \times 10^3}$$

$$i = 10 \times 10^{-3} \text{ A}$$

$$v(t) = 20k i = (20 \times 10^3)(10 \times 10^{-3}) = 200 \text{ V}$$

$$v(0^+) = 200 \text{ V}$$

(b)  $t > 0$

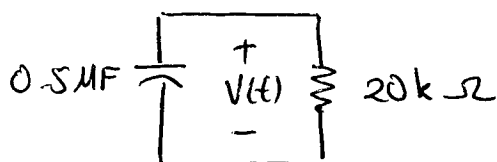

$$\tau = RC = (20 \times 10^3)(0.5 \times 10^{-6}) = 0.01 \text{ s}$$

$$\tau = 10 \text{ ms}$$

$$\begin{aligned}
 (c) \quad v(t) &= K e^{-t/RC} \quad \checkmark \quad t > 0 \\
 v(t) &= K e^{-t/0.01} \quad \checkmark \quad t > 0 \\
 v(t) &= K e^{-100t} \quad \checkmark \quad t > 0
 \end{aligned}$$

$$v(0^+) = v(0^-) = 200 = K e^{-0} \Rightarrow K = 200$$

$$v(t) = 200 e^{-100t} \quad \checkmark \quad t > 0$$

$$\begin{aligned}
 (d) \quad W_0 &= \frac{1}{2} C v(0)^2 \\
 &= \frac{1}{2} (0.5 \times 10^{-6}) (200)^2 \\
 &= 0.01 \\
 &= 10 \text{ mJ}
 \end{aligned}$$

$$\begin{aligned}
 (e) \quad W_0 - 0.75 W_0 &= \frac{1}{2} C v(t)^2 \\
 10 \times 10^{-3} - 0.75 \times 10 \times 10^{-3} &= \frac{1}{2} (0.5 \times 10^{-6}) (200 e^{-100t})^2 \\
 2.5 \times 10^{-3} &= 10 \times 10^{-3} e^{-200t} \\
 e^{-200t} &= 0.25
 \end{aligned}$$


$$\ln(e^{-200t}) = \ln(0.25)$$

$$-200t = \ln(0.25)$$

$$t = \frac{\ln(0.25)}{-200}$$


$$t = 6.93 \text{ ms}$$

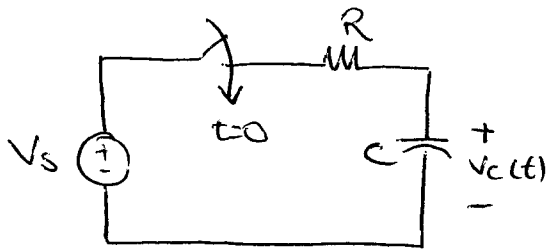Charging a capacitor from a DC source  
Consider the following circuit.



We assume that  $V_c(0^-) = V_i$

$t \geq 0$

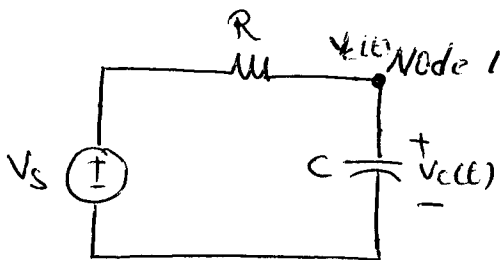

KCL at node 1:

$$C \frac{dV_c(t)}{dt} + \frac{V_c(t) - V_s}{R} = 0$$

$$RC \frac{dV_c(t)}{dt} + V_c(t) = V_s \quad (1)$$

The above equation's solution:

$$V_c(t) = K_1 + K_2 e^{st} \quad (2)$$

in which  $K_1, K_2$  and  $s$  are constants to be determined.

Substitute (2) into (1)

$$RC \frac{d}{dt} (K_1 + K_2 e^{st}) + (K_1 + K_2 e^{st}) = V_s$$

$$RC K_2 s e^{st} + K_1 + K_2 e^{st} = V_s$$

$$\underbrace{(RCs+1)}_0 K_2 e^{st} + K_1 = V_s$$

$$RCs+1=0 \Rightarrow s = -1/RC$$

$$K_1 = V_s$$

$$V_c(t) = V_s + K_2 e^{-t/RC}$$

Now we use initial conditions ( $V_c(0^-) = V_i$ ) to find  $K_2$ .

$$V_c(0^+) = V_c(0^-) = V_i = V_s + K_2 e^{-0/RC}$$

$$V_s + K_2 = V_i$$


$$K_2 = V_i - V_s$$

$$V_c(t) = V_s + (V_i - V_s) e^{-t/RC} \quad t > 0$$

$$\text{If } V_c(0^+) = V_c(0^-) = 0$$

$$V_c(t) = V_s - V_s e^{-t/RC} \quad t > 0$$

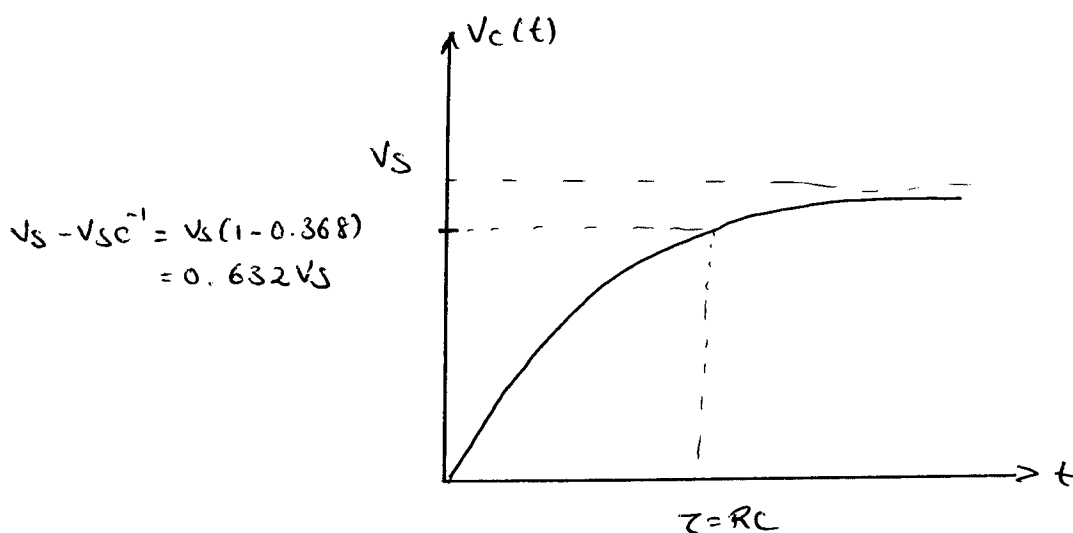
The second term on the right-hand side is called the transient response. The first term on the right hand side is steady-state response.






P4.5

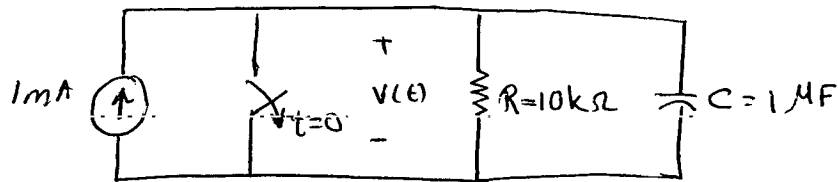The switch for the following circuit opens at  $t=0$ . Find an expression for  $v(t)$  and sketch to scale versus time.




Solution:

$t < 0$

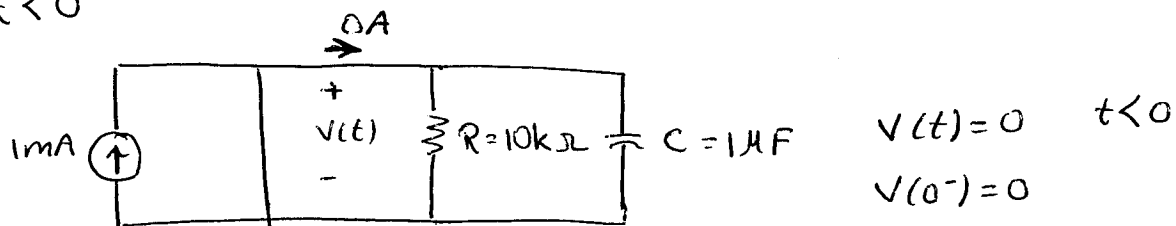

$t > 0$

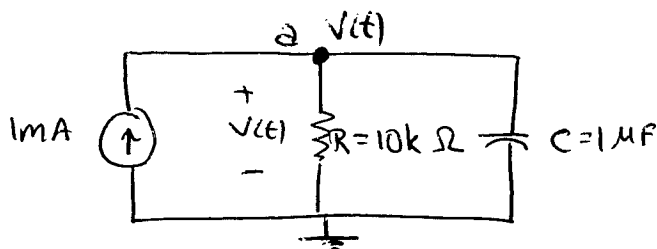

KCL at node a:

$$\frac{v(t)}{R} + C \frac{dv(t)}{dt} - 1 \times 10^{-3} = 0$$

$$RC \frac{dv(t)}{dt} + v(t) = 1 \times 10^{-3} R$$

$$(10 \times 10^3)(1 \times 10^{-6}) \frac{dv(t)}{dt} + v(t) = (1 \times 10^{-3})(10 \times 10^3)$$

$$0.01 \frac{dv(t)}{dt} + v(t) = 10 \quad (1)$$

$$v(t) = K_1 + K_2 e^{st}$$

$$S = \frac{-1}{Rc}$$

$$S = \frac{-1}{(10 \times 10^3)(1 \times 10^{-6})}$$

$$S = -100$$

$$V(t) = K_1 + K_2 e^{-100t} \quad (2)$$

Substitute (2) into (1)

$$0.01 \frac{d}{dt} (K_1 + K_2 e^{-100t}) + (K_1 + K_2 e^{-100t}) = 10$$

$$0.01 (K_2)(-100) e^{-100t} + K_1 + K_2 e^{-100t} = 10$$

$$-K_2 e^{-100t} + K_1 + K_2 e^{-100t} = 10$$


$$K_1 = 10$$

$$V_c(t) = 10 + K_2 e^{-100t}$$

$$V_c(0^+) = V_c(0^-) = 0 = 10 + K_2 e^{-0}$$

$$K_2 = -10$$
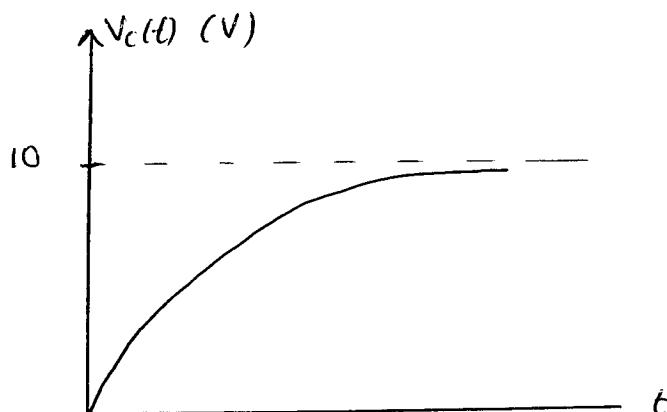
$$V_c(t) = 10 - 10 e^{-100t} \quad \checkmark \quad t \geq 0$$



## DC Steady State

The response that exist a long time after the switch has taken place is called the steady-state response. For DC sources, the steady state current and voltages are constant.

Current through a capacitance

$$i_c(t) = C \frac{dv_c(t)}{dt}$$

$$\text{If } v_c(t) = \text{constant}, \quad i_c(t) = 0$$

For steady state conditions with dc sources, capacitances behaves as open circuits.


Similarly for an inductance

$$v_L(t) = L \frac{di_L(t)}{dt}$$

$$\text{If } i_L(t) = \text{constant}, \quad v_L(t) = 0$$


For steady state conditions with dc sources, inductances behaves as short circuit.

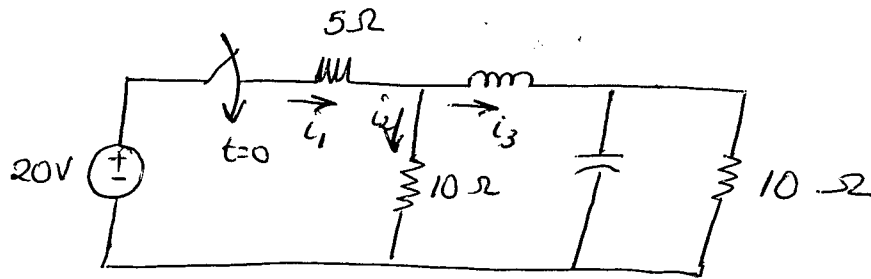Exercise: Find  $i_1$ ,  $i_2$  and  $i_3$  for  $t \gg 0$ .



Solution:

$t \gg 0$  : steady state

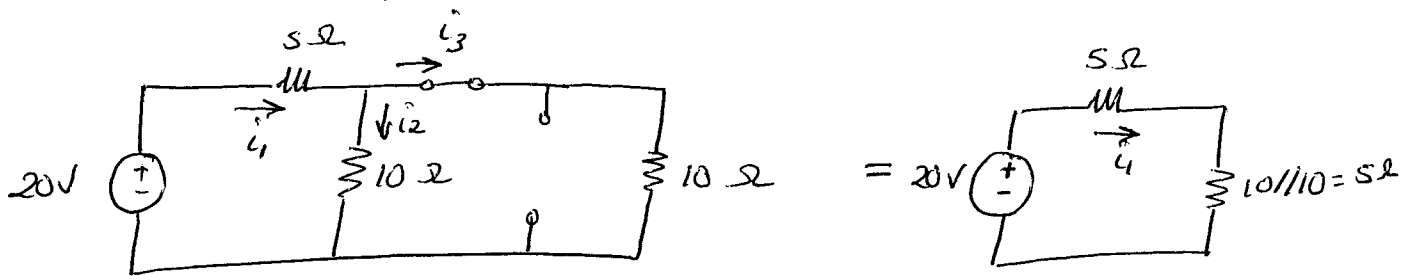

$$i_1 = \frac{20}{10} = 2 \text{ A}$$

$$i_2 = i_1 \frac{10}{10+10} =$$

$$= 2 \frac{10}{20}$$


$$= 1 \text{ A}$$

$$i_3 = 2 \frac{10}{10+10}$$


$$= 2 \frac{10}{20}$$

$$= 1 \text{ A}$$

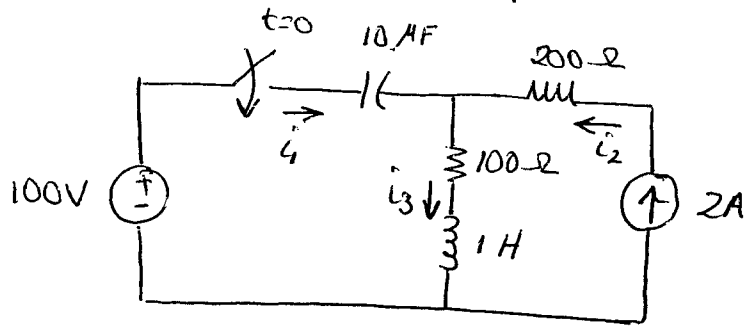P4.10 Find the steady state values of  $i_1$ ,  $i_2$  and  $i_3$ .



Solution:

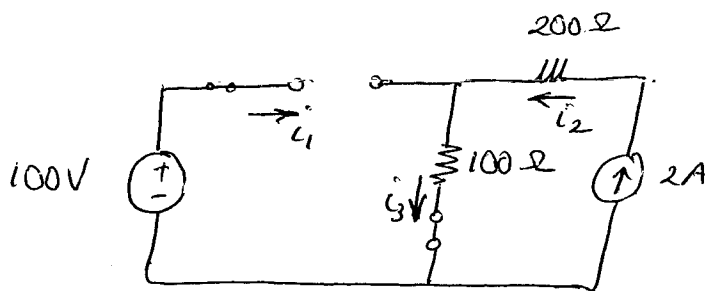


$$i_1 = 0$$

$$i_2 = i_3 = 2 \text{ A}$$

## RL Circuits


Consider the following circuit

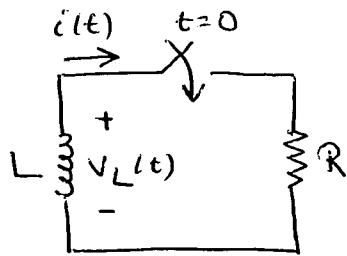

Assume that

$$i(0^-) = i_0$$

$t > 0$

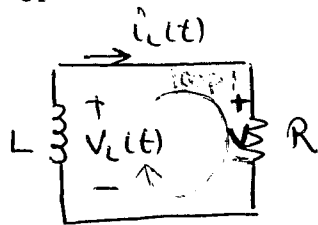

KVL for loop 1:

$$-V_L(t) + V = 0$$

$$V_L(t) = -L \frac{di_L(t)}{dt}$$

$$V = Ri_L(t)$$

$$L \frac{di_L(t)}{dt} + Ri_L(t) = 0$$

$$\frac{L}{R} \frac{di_L(t)}{dt} + i_L(t) = 0 \quad (1)$$

The solution of (1):

$$i_L(t) = Ke^{st} \quad (2)$$

in which  $K$  and  $s$  are constants to be determined.

Substitute (2) into (1)

$$\frac{L}{R} \frac{d}{dt} (K e^{st}) + K e^{st} = 0$$

$$\frac{L}{R} K s e^{st} + K e^{st} = 0$$

$$\left( \frac{L}{R} s + 1 \right) \underbrace{K e^{st}}_{\neq 0} = 0$$

$$\frac{L}{R} s + 1 = 0$$

$$s = -\frac{R}{L} \Rightarrow \tau = \frac{L}{R} \quad \text{Time constant of inductor}$$


$$i_L(t) = K e^{-tR/L}$$


The inductor current must be continuous

$$i_L(0^+) = i_L(0^-) = i_0 = K e^{-0}$$

$$K = i_0$$
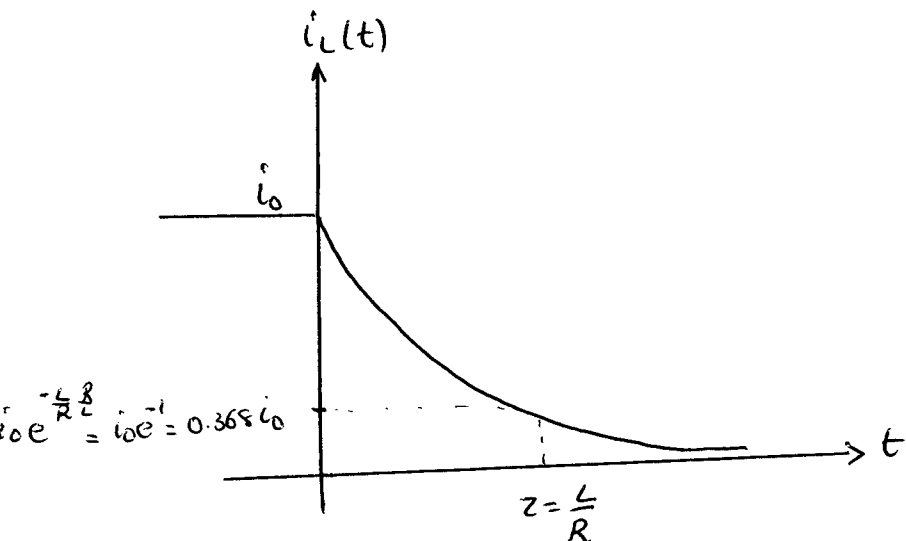
$$i_L(t) = i_0 e^{-tR/L} \quad A, \quad t > 0$$




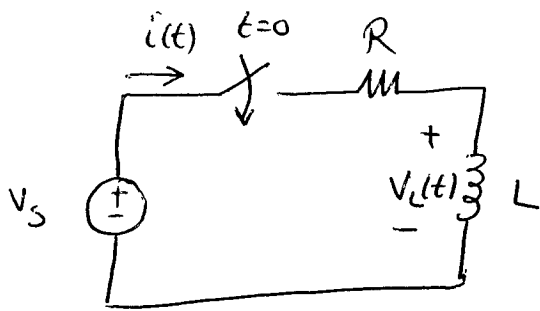

We assume that  $i(t) = 0$ ,  $t < 0$

After the switch is closed, the current increases in value eventually reaching a steady-state value.

$t > 0$

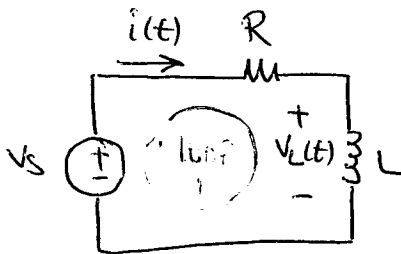

KVL for loop 1:

$$-V_s + Ri(t) + V_L(t) = 0 \quad (1)$$

$$V_L(t) = L \frac{di(t)}{dt} \quad (2)$$

Substitute (2) into (1)

$$-V_s + Ri(t) + L \frac{di(t)}{dt} = 0$$

$$\frac{L}{R} \frac{di(t)}{dt} + i(t) = \frac{V_s}{R} \quad (3)$$

The above equation's solution:

$$i(t) = K_1 + K_2 e^{st} \quad (4)$$



Substitute (4) into (3)

$$\frac{L}{R} \frac{d}{dt} (K_1 + K_2 e^{st}) + (K_1 + K_2 e^{st}) = \frac{V_s}{R}$$

$$\frac{L}{R} K_2 s e^{st} + K_1 + K_2 e^{st} = \frac{V_s}{R}$$

$$K_1 + \left( \frac{L s + 1}{R} \right) K_2 e^{st} = \frac{V_s}{R}$$

$$\frac{L}{R} s + 1 = 0 \Rightarrow s = -\frac{R}{L}$$

$$K_1 = \frac{V_s}{R}$$

$$i(t) = \frac{V_s}{R} + K_2 e^{-tR/L}$$

Now we use initial conditions ( $i(0) = i_0$ ) to find  $K_2$


$$i(0^+) = i(0^-) = i_0 = \frac{V_s}{R} + K_2 e^{-0}$$

$$K_2 = i_0 - \frac{V_s}{R}$$

$$i(t) = \frac{V_s}{R} + \left( i_0 - \frac{V_s}{R} \right) e^{-tR/L} \quad t > 0$$


$$\text{If } i(0^+) = i(0^-) = 0$$
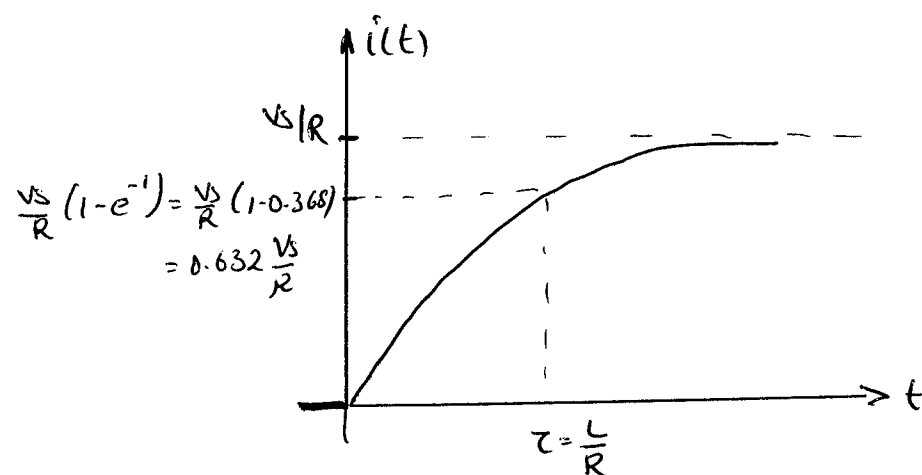
$$i(t) = \frac{V_s}{R} - \frac{V_s}{R} e^{-tR/L} \quad t > 0$$




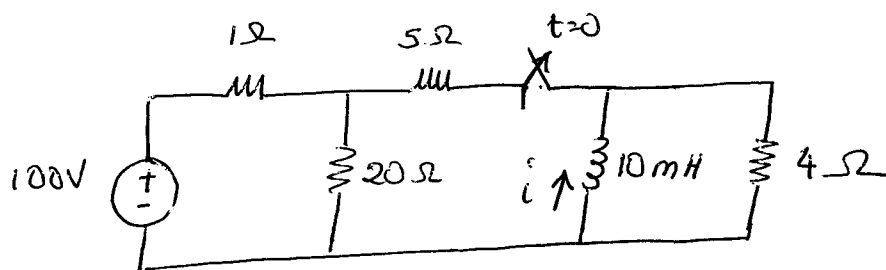
Question: The switch for the following circuit has been closed for a long time and is opened at  $t=0$

- Calculate the initial value of  $i$ .
- What is the initial energy stored in the inductor?
- What is the time constant of the circuit for  $t > 0$ ?
- What is  $i(t)$  for  $t \geq 0$ ?
- What percentage of the initial energy stored has been dissipated in  $4\Omega$  resistor 5ms after the switch has been opened?



Solution:

(a)  $i(0) = ?$

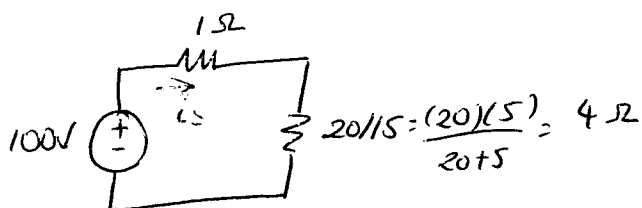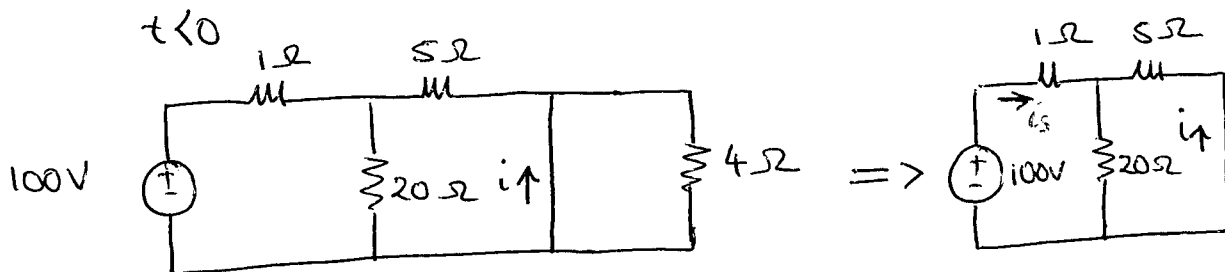


$$i_s = \frac{100}{1+4} = 20 \text{ A}$$

$$i = -i_s \cdot \frac{20}{20+5} = -20 \cdot \frac{20}{20+5} = -16 \text{ A}$$

$$i(0) = -16 \text{ A}$$

$$\begin{aligned}
 (b) \quad \omega_0 &= \frac{1}{2} L \hat{i}(0)^2 \\
 &= \frac{1}{2} (10 \times 10^{-3}) (-16)^2 \\
 &= 1.28 \text{ J}
 \end{aligned}$$

$$(c) \quad t > 0$$

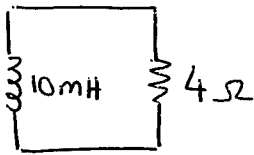

$$\tau = \frac{L}{R} = \frac{10 \times 10^{-3}}{4} = 2.5 \times 10^{-3} = 2.5 \text{ ms}$$

$$(d) \quad \hat{i}(t) = \hat{i}_0 e^{-tR/L}$$

$$\hat{i}(t) = -16 e^{-t/2.5 \times 10^{-3}}$$

$$\hat{i}(t) = -16 e^{-400t} \text{ A} \quad t \geq 0$$

$$(e) \quad \omega(t) = \frac{1}{2} L \hat{i}(t)^2$$

$$\begin{aligned}
 \omega(5 \times 10^{-3}) &= \frac{1}{2} (10 \times 10^{-3}) \hat{i}(5 \times 10^{-3})^2 \\
 &= \frac{1}{2} (10 \times 10^{-3}) (-16 e^{-400(5 \times 10^{-3})})^2 \\
 &= \frac{1}{2} (10 \times 10^{-3}) (-2.165)^2 \\
 &= 0.0234 \text{ J}
 \end{aligned}$$

$\omega_0$	$\omega(5 \times 10^{-3})$
100	$x$


$$x = \frac{100 \times \omega(5 \times 10^{-3})}{\omega_0} = \frac{100 \times 0.0234}{1.28} = 1.83 \%$$

$$\text{Dissipated} = 100 - 1.83 = 98.17 \%$$
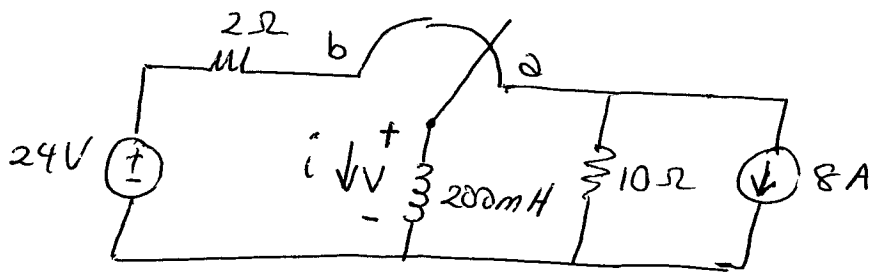
# Home Exercise:


The switch in the circuit has been in position a for a long time. At  $t=0$ , the switch moves from position a to position b.

- Find the expression for  $i(t)$  for  $t \geq 0$ .
- What is the initial voltage across the inductor just after the switch has been moved to position b?
- How many milliseconds after the switch has been moved to position b does the inductor voltage equal  $24\text{ V}$ ?




Solution:

(a)  $t < 0$

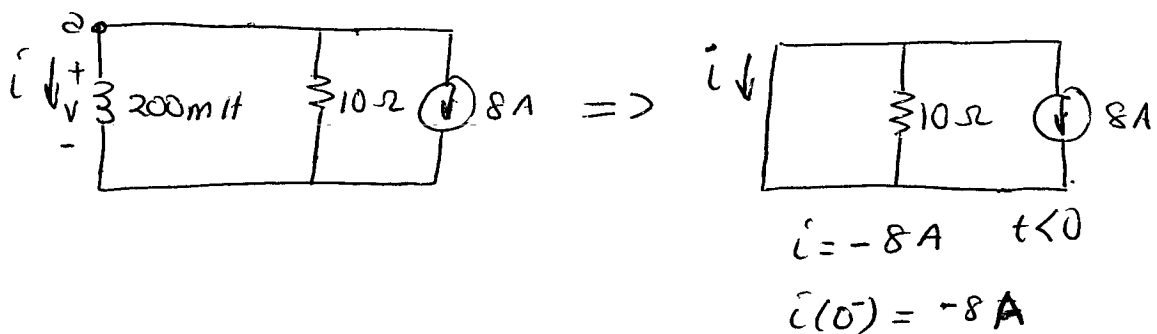

(b)  $t > 0$

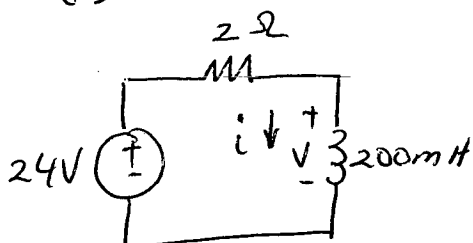

$$i(t) = \frac{V_s}{R} + \left( i(0^+) - \frac{V_s}{R} \right) e^{-tR/L} \quad A \quad t \geq 0$$

$$= \frac{24}{2} + \left( -8 - \frac{24}{2} \right) e^{-t \cdot 2 / 200 \times 10^{-3}} \quad A \quad t \geq 0$$

$$= 12 + (-8 - 12) e^{-10t} \quad A \quad t \geq 0$$

$$= 12 - 20 e^{-10t} \quad A \quad t \geq 0$$

$$(b) \quad v(t) = L \frac{di(t)}{dt}$$

$$= (200 \times 10^{-3}) \frac{d}{dt} (12 - 20 e^{-10t}) \quad V, t \geq 0$$

$$= (200 \times 10^{-3}) (-20)(-10) e^{-10t} \quad V, t \geq 0$$

$$= 40 e^{-10t} \quad V, t \geq 0$$

$$v(0^+) = 40 e^{-10(0)} = 40 \text{ V}$$

$$(c) \quad v(t) = 40 e^{-10t} \text{ V} \quad t \geq 0$$

$$24 = 40 e^{-10t}$$

$$e^{-10t} = \frac{24}{40}$$

$$\ln(e^{-10t}) = \ln\left(\frac{24}{40}\right)$$


$$-10t(\ln e) = \ln\left(\frac{24}{40}\right)$$

$$t = \frac{\ln(24/40)}{-10}$$

$$t = 51.08 \text{ ms}$$


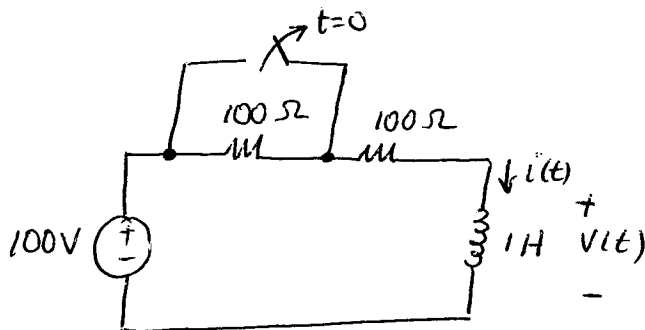
### Exercise 4-6

consider the following circuit. Assume that the switch has been closed for a very long time prior to  $t=0$ . Find expressions for  $i(t)$  and  $v(t)$ .



Solution:



$t < 0$

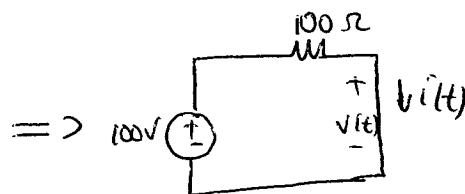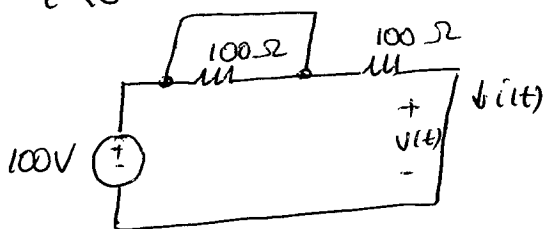

$$i(t) = \frac{100}{100} = 1 \text{ A } t < 0$$

$$v(t) = 0 \text{ V } t < 0$$

$t > 0$

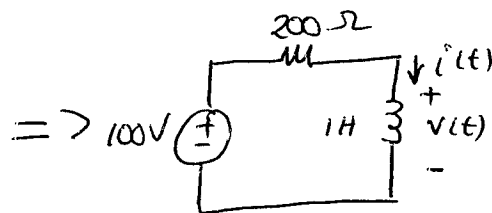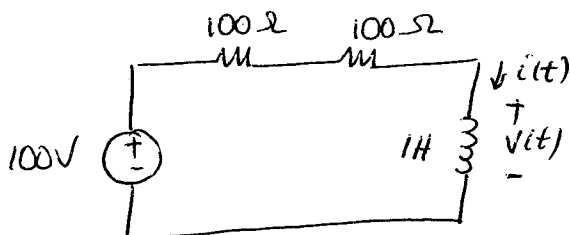

$$i(t) = \frac{V_s}{R} \left( 1 - \frac{V_s}{R} \right) e^{-tR/L} \quad \text{A, } t \geq 0$$

$$= \frac{100}{200} \left( 1 - \frac{100}{200} \right) e^{-t200/1}$$

$$= 0.5 + 0.5 e^{-200t} \quad \text{A } t \geq 0$$


$$\begin{aligned}
 v(t) &= L \frac{di(t)}{dt} \\
 &= 1 \frac{d}{dt} (0.5 + 0.5 e^{-200t}) \\
 &= +0.5(-200) e^{-200t} \\
 &= -100 e^{-200t} \quad \text{V} \quad t \geq 0
 \end{aligned}$$

$$i(t) = \begin{cases} 1 \text{ A} & , t < 0 \\ 0.5 + 0.5 e^{-200t} \text{ A} & , t \geq 0 \end{cases}$$

$$v(t) = \begin{cases} 0 \text{ V} & , t < 0 \\ -100 e^{-200t} \text{ V} & , t \geq 0 \end{cases}$$

## RC and RL Circuits with General Sources

Consider the following circuit.

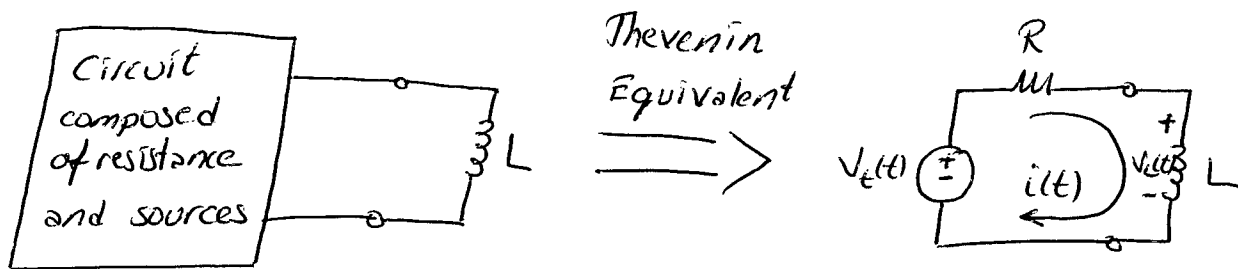

$$\text{KVL : } -V_t(t) + Ri(t) + V_L(t) = 0$$

$$V_L(t) = L \frac{di(t)}{dt}$$

$$-V_t(t) + Ri(t) + L \frac{di(t)}{dt} = 0$$

$$\frac{L}{R} \frac{di(t)}{dt} + i(t) = \frac{V_t(t)}{R}$$

In general, the equation for any circuit containing one inductance or one capacitance can be put into the form

$$\tau \frac{dx(t)}{dt} + x(t) = f(t)$$

Time constant                      Forcing function

(If we have a circuit without sources  $f(t)=0$ . For DC sources  $f(t)=\text{constant}$ )

Solution of the differential equation:

General solution consists two parts :  $x(t) = x_p(t) + x_c(t)$

(1) Particular solution (force response)  $x_p(t)$  is any expression that satisfies

$$\tau \frac{dx_p(t)}{dt} + x_p(t) = f(t)$$



(2) Complementary solution (Natural response)  $x_c(t)$  is the solution of the homogeneous equation

$$\tau \frac{dx_c(t)}{dt} + x_c(t) = 0$$

$$\frac{dx_c(t)/dt}{x_c(t)} = -\frac{1}{\tau}$$

Integrating both sides

$$\int \frac{dx_c(t)}{x_c(t)} = \int -\frac{1}{\tau} dt$$

$$\ln(x_c(t)) = -\frac{t}{\tau} + C \leftarrow \text{the constant of integration}$$

$$x_c(t) = e^{(-\frac{t}{\tau} + C)}$$


$$= e^C e^{-t/\tau} \quad K = e^C$$

$$= K e^{-t/\tau}$$

Step-by-step solution


- 1- Write the circuit equation and reduce it to a first order differential equation.
- 2- Find a particular solution depending on the form of forcing function
- 3- Obtain the complete solution by adding the particular solution to the complementary solution which contains the arbitrary constant
- 4- Use initial conditions to find  $K$ .

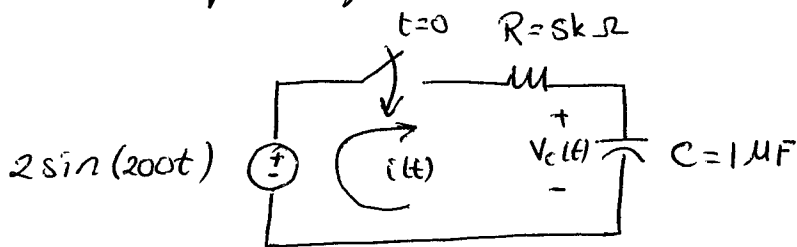Example: Solve for the current in the following circuit. The capacitor is initially charged so that  $V_c(0^+) = 1V$



Solution:

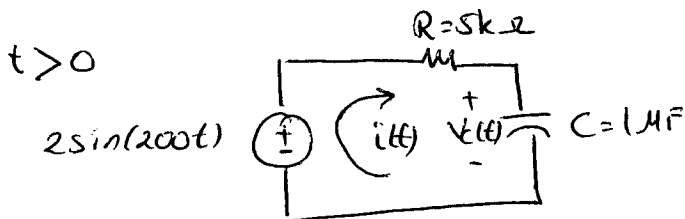step 1: Obtain first order derivative equation.



$$\text{KVL: } -2\sin(200t) + Ri(t) + V_c(t) = 0 \quad (1)$$

$$V_c(t) = \frac{1}{C} \int_0^t i(t) dt + V_c(0) \quad (2)$$

Substitute (2) into (1)

$$-2\sin(200t) + Ri(t) + \frac{1}{C} \int_0^t i(t) dt + V_c(0) = 0 \quad (3)$$

Take the derivative of each term in (3)

$$-2(200)\cos(200t) + R \frac{di(t)}{dt} + \frac{1}{C} i(t) = 0$$

$$RC \frac{di(t)}{dt} + i(t) = 400 C \cos(200t)$$

$$(5 \times 10^3)(1 \times 10^{-6}) \frac{di(t)}{dt} + i(t) = (400) \times (1 \times 10^{-6}) \cos(200t)$$

$$5 \times 10^{-3} \frac{di(t)}{dt} + i(t) = 400 \times 10^{-6} \cos(200t) \quad (4)$$

Step 2: Find  $i_p(t)$

Since the derivatives of  $\sin(200t)$  and  $\cos(200t)$  are  $200 \cos(200t)$  and  $-200 \sin(200t)$  respectively we try a particular solution of the form

$$i_p(t) = A \cos(200t) + B \sin(200t) \quad (5)$$

Substitute (5) into (4)

$$5 \times 10^{-3} \frac{d}{dt} (A \cos(200t) + B \sin(200t)) + A \cos(200t) + B \sin(200t) = 400 \times 10^{-6} \cos(200t)$$

$$5 \times 10^{-3} (-A 200 \sin(200t) + B 200 \cos(200t)) + A \cos(200t) + B \sin(200t) = 400 \times 10^{-6} \cos(200t)$$

$$(-A + B) \sin(200t) + (B + A) \cos(200t) = 400 \times 10^{-6} \cos(200t) \quad (6)$$

LHS should be equal to RHS for (6)

$$-A + B = 0$$

$$B + A = 400 \times 10^{-6}$$

$$\begin{array}{r} + \\ \hline 2B = 400 \times 10^{-6} \end{array} \Rightarrow B = 200 \times 10^{-6} = 200 \mu A$$

$$A = 200 \mu A$$

Substitute A and B in (5)

$$i_p(t) = 200 \cos(200t) + 200 \sin(200t) \mu A$$

Step 3: Find  $\hat{i}_c(t)$  and add it to  $\hat{i}_p(t)$

$$RC \frac{d\hat{i}_c(t)}{dt} + \hat{i}_c(t) = 0$$


$$\hat{i}_c(t) = K e^{-t/RC}$$

$$\hat{i}(t) = \hat{i}_p(t) + \hat{i}_c(t)$$

$$= 200 \cos(200t) + 200 \sin(200t) + K e^{-t/RC}$$

Step 4: Find  $K$  by initial conditions.

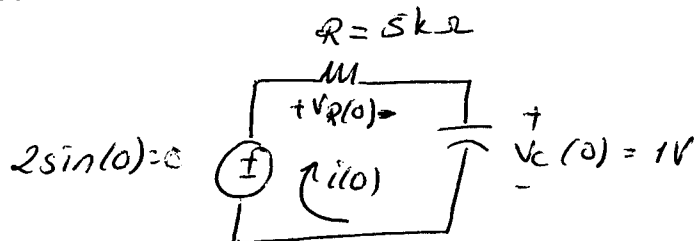The voltages and currents immediately after the switch closes are shown below.



$$KVL: V_R(0^+) + V_C(0) - 0 = 0$$

$$V_R(0^+) = -V_C(0^+) = -1$$

$$i(0^+) = \frac{V_R(0^+)}{R} = \frac{-1}{5000} = -200 \mu A$$


$$i(0^+) = -200 = 200 \cos(200(0)) + 200 \sin(200(0)) + K e^{-0}$$

$$-200 = 200 + K$$

$$K = -400 \mu A$$


$$i(t) = 200 \cos(200t) + 200 \sin(200t) - 400 e^{-t/RC} \mu A$$

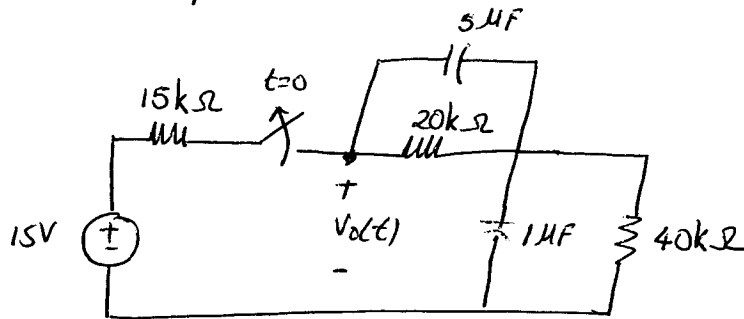Question: The switch in the following circuit has been closed for a long time before being opened at  $t=0$ . Find  $V_o(t)$  for  $t \geq 0$ .



Solution:

$t \geq 0$

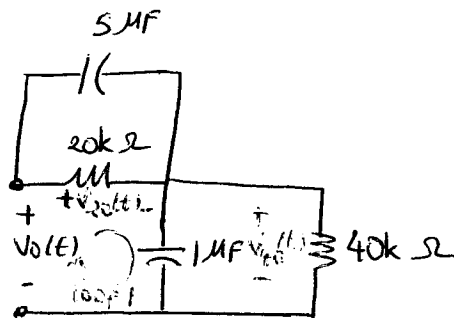

KVL for loop 1:

$$-V_o(t) + V_{20}(t) + V_{40}(t) = 0 \quad t \geq 0$$


$$V_o(t) = V_{20}(t) + V_{40}(t)$$

$$V_{20}(t) = V_{20}(0) e^{-t/(5 \times 10^{-6})(20 \times 10^3)} = V_{20}(0) e^{-10t} \quad t \geq 0$$

$$V_{40}(t) = V_{40}(0) e^{-t/(1 \times 10^{-6})(40 \times 10^3)} = V_{40}(0) e^{-25t} \quad t \geq 0$$

$$V_o(t) = V_{20}(0) e^{-10t} + V_{40}(0) e^{-25t} \quad t \geq 0$$

$t < 0$

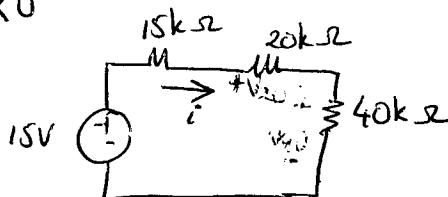



$$\hat{i} = \frac{15}{(15 + 20 + 40) \times 10^3} = 0.2 \text{ mA}$$

$$V_{20} = 20k\hat{i} = (20k)(0.2m) = 4V \Rightarrow V_{20}(0) = 4V$$

$$V_{40} = 40k\hat{i} = (40k)(0.2m) = 8V \Rightarrow V_{40}(0) = 8V$$

$$V_o(t) = 4e^{-10t} + 8e^{-25t} \quad t \geq 0$$

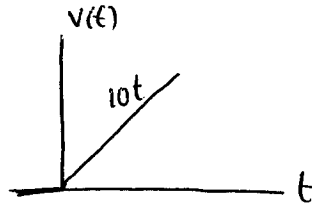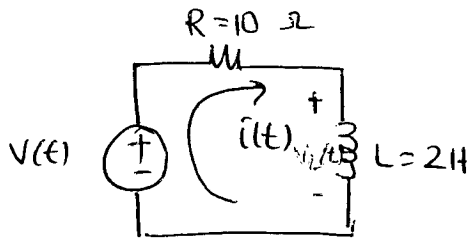P4.23 The voltage source shown below is called a ramp function. Assume that  $i(0)=0$ . Write the differential equation for  $i(t)$  and find the complete solution. (Hint: Try  $i_p(t)=A+Bt$ )



Solution:

$$\text{KVL: } -V(t) + Ri(t) + v_L(t) = 0$$

$$v_L(t) = L \frac{di(t)}{dt}$$

$$-V(t) + Ri(t) + L \frac{di(t)}{dt} = 0$$

$$\frac{L}{R} \frac{di(t)}{dt} + i(t) = \frac{V(t)}{R}$$

$$\frac{2}{10} \frac{di(t)}{dt} + i(t) = \frac{10t}{10}$$

$$0.2 \frac{di(t)}{dt} + i(t) = t \quad (1)$$

$$i(t) = i_p(t) + i_c(t)$$

$$i_p(t) = A + Bt \quad (2)$$

Substitute (2) into (1)

$$0.2 \frac{d}{dt}(A+Bt) + (A+Bt) = t$$

$$0.2 B + A + Bt = t$$

$$0.2 B + A = 0$$

$$B = 1 \Rightarrow A = -0.2$$

$$i_p(t) = -0.2 + t$$

$$\hat{i}_c(t) = K e^{-tR/L}$$

$$\hat{i}_c(t) = K e^{-t/0.2}$$

$$\hat{i}_c(t) = K e^{-5t}$$

$$\hat{i}(t) = \hat{i}_p(t) + \hat{i}_c(t)$$

$$\hat{i}(t) = -0.2 + t + K e^{-5t}$$

$$\hat{i}(0^+) = \hat{i}(0^-) = 0 = -0.2 + 0 + K e^{-0}$$


$$K = 0.2$$

$$\hat{i}(t) = -0.2 + t + 0.2 e^{-5t} \quad A \quad t > 0$$

$$\hat{i}(t) = \begin{cases} 0 A & , t < 0 \\ -0.2 + t + 0.2 e^{-5t} \quad A & , t > 0 \end{cases}$$

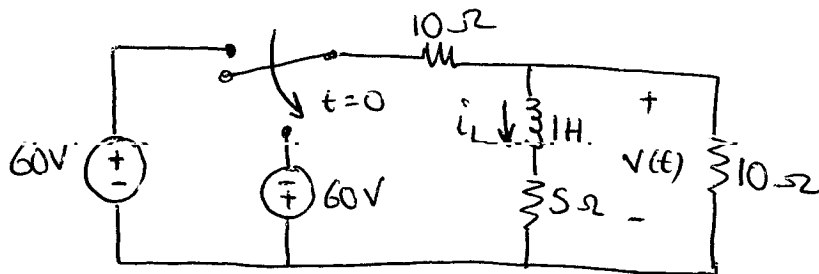
Question: (midterm II - 1996)

The circuit is in steady state at  $t=0^-$ . The switch changes position at  $t=0$ . Find  $i_L(t)$  for  $t>0$ . and  $v(t)$  for  $t>0$ .



Solution:


$t < 0$

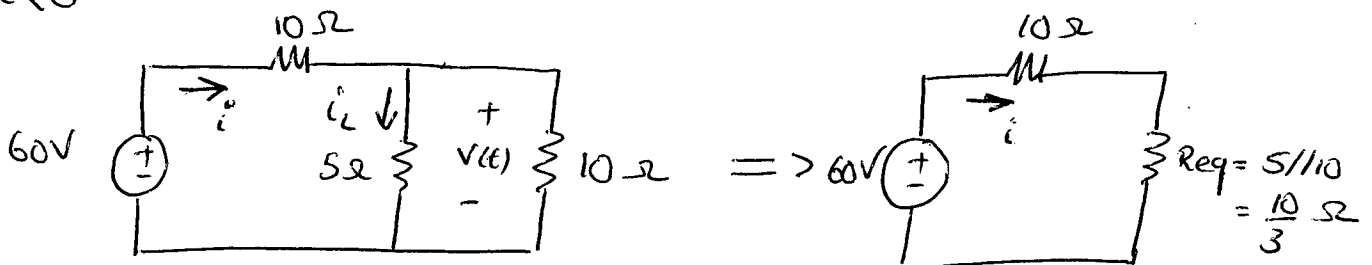

$$i = \frac{60}{10 + \frac{10}{3}} = 4.5 \text{ A}$$


$$i_L = i \frac{10}{10+5} = 4.5 \frac{10}{15} = 3 \text{ A} \quad t < 0 \Rightarrow i_L(0) = 3 \text{ A}$$

$t > 0$

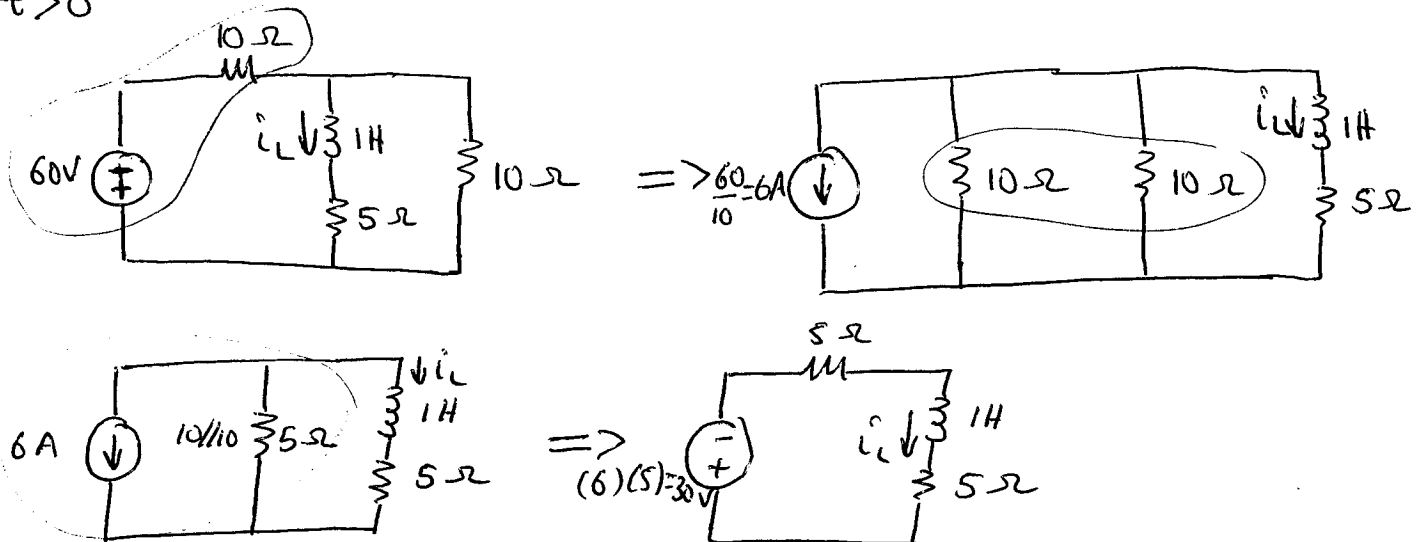



$$5 + 5 = 10 \Omega$$

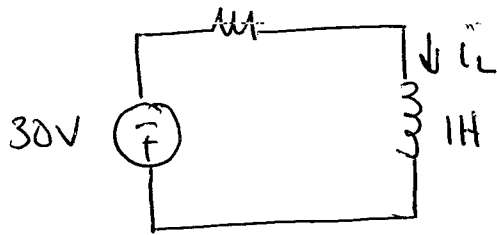


$$i_L(t) = \frac{V_s}{R} + \left( i_L(0) - \frac{V_s}{R} \right) e^{-tR/L} \quad A$$

$$i_L(t) = \frac{-30}{10} + \left( 3 - \left( \frac{-30}{10} \right) \right) e^{-t10/1}$$

$$i_L(t) = -3 + (3 + 3)e^{-10t}$$
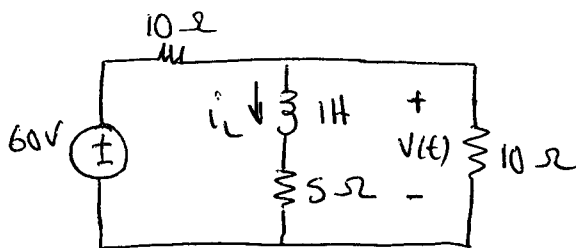
$$i_L(t) = -3 + 6e^{-10t} \quad A, \quad t > 0$$



$$V(t) = V_L(t) + V_R(t)$$

$$= L \frac{di_L(t)}{dt} + 5i_L(t)$$

$$= 1 \frac{d}{dt} (-3 + 6e^{-10t}) + 5(-3 + 6e^{-10t})$$

$$= -60e^{-10t} - 15 + 30e^{-10t}$$

$$= -15 - 30e^{-10t} \quad V, \quad t > 0$$