

***Binary Parallel Adder / Subtractor:***

Ex: Design a 4-bit parallel adder/subtractor with an  $S$  control input.

When  $S = 1 \Rightarrow$  parallel subtractor

When  $S = 0 \Rightarrow$  parallel adder

